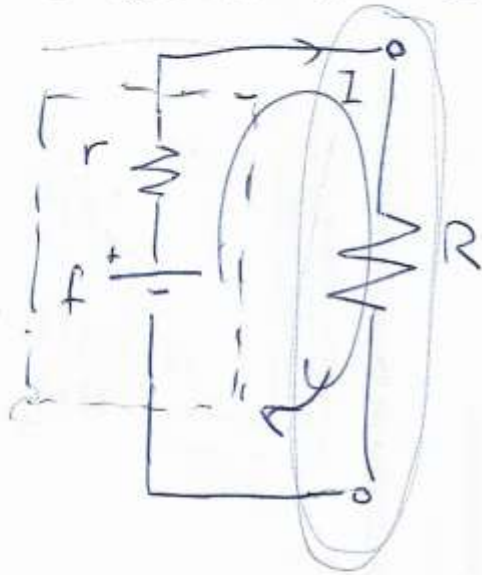


ESERCITAZIONE 12/03/2020

CIRCUITI IN REGIME STAZIONARIO



carico (load)

$$\sum_i f_i = \sum_j R_j I_j$$

$$f = rI + RI = (r+R)I$$

$$I = f / (r+R)$$


$$P = RI^2 = R \left(\frac{f}{r+R} \right)^2 > \phi$$

$$\frac{dP}{dR} = f^2 \cdot \frac{(r+R)^2 - 2R(r+R)}{(r+R)^4} = \dots = \frac{r^2 - R^2}{(r+R)^4}$$

$$= \frac{r-R}{(r+R)^3} = \phi \quad R=r$$

$$P = rI^2 = \frac{f^2}{4r}$$
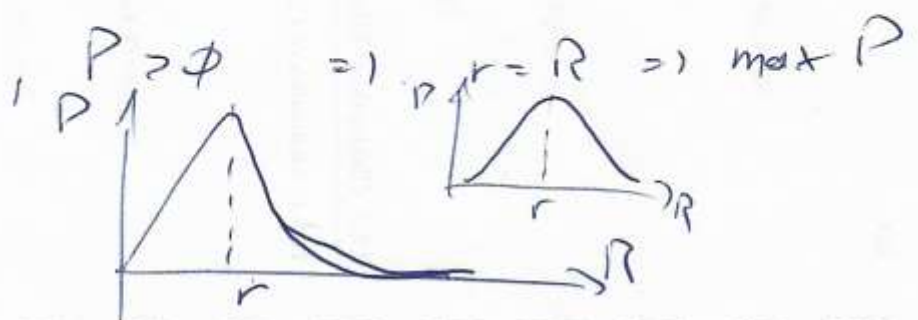
$$\lim_{\substack{R \rightarrow \phi \\ R \rightarrow +\infty}} P = \phi$$




$$\eta = \frac{P_R}{P_T} = \frac{P_R}{P_R + P_r} = \frac{R I^2}{(r+R) I^2} = \frac{R}{r+R}$$

~~$$\eta = 1$$~~

$$R \rightarrow +\infty \Rightarrow P_R = P$$

$$P_{\text{max}} \Rightarrow R = r \Rightarrow \eta = 50\%$$

Ponte di Wheatstone R_x incognita

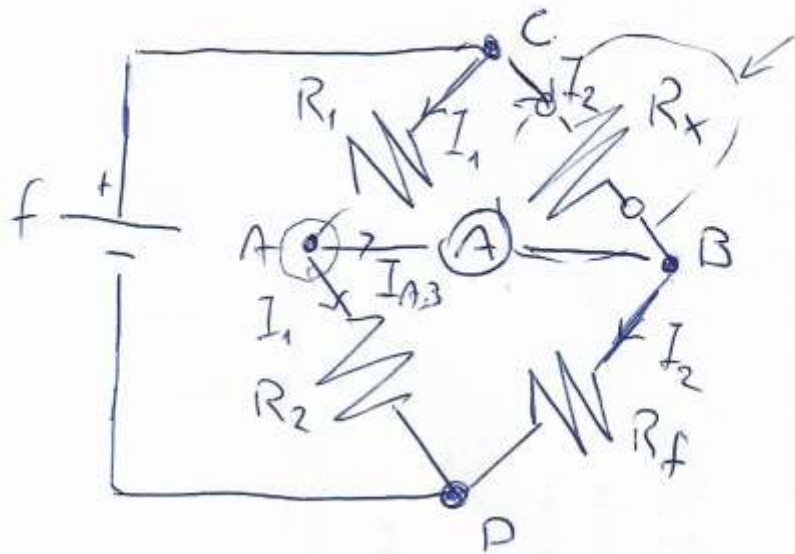

R_1, R_2 variabili
 R_f fissa

$$I_{AB} = \phi \quad \Delta V_{AB} = V_A - V_B = \phi$$


$$V_C - V_A = V_C - V_B \rightarrow R_1 I_1 = R_x I_2$$

$$V_A - V_D = V_B - V_D \quad \overline{R_2 I_1 = R_f I_2}$$

$$\frac{R_1}{R_2} = \frac{R_x}{R_f} \Rightarrow \boxed{R_x = \frac{R_1}{R_2} R_f}$$



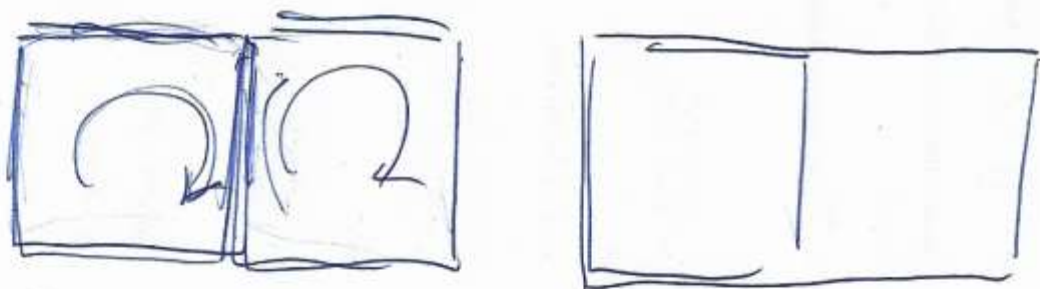
① $\# \text{ maglie indipendenti} = \# \text{ rami} - \# \text{ nodi} + 1$



② Assegnare versi alle correnti di maglia

③ Kirchhoff eq. alle maglie (+ eq. ai nodi)

④ Risolvere \rightarrow correnti...

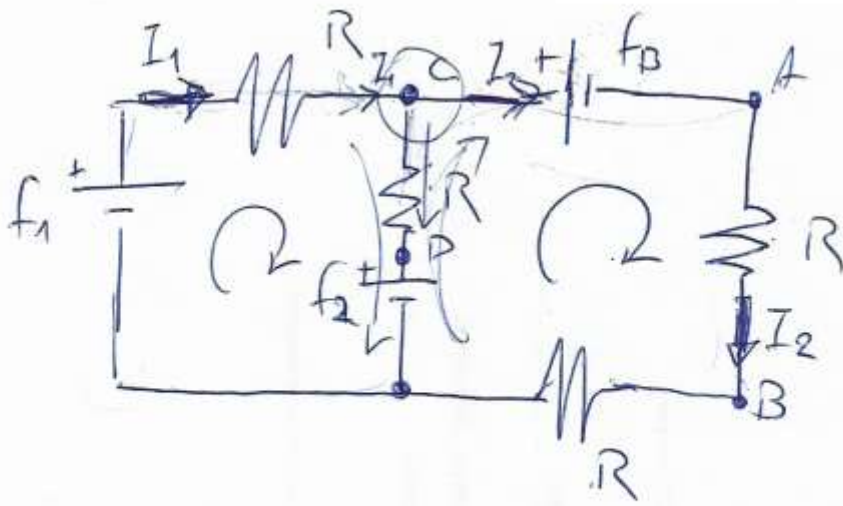

$$\Delta V_{AB} = ?$$

$$\Delta V_{CD} = ?$$

$$f_1 = 12 \text{ V}$$

$$f_2 = 3 \text{ V}$$

$$f_3 = 5 \text{ V}$$

$$R = 1 \text{ k}\Omega$$

$$\begin{cases} f_1 - f_2 = RI_1 + R(I_1 - I_2) \\ f_2 - f_3 = R(I_2 - I_1) + 2RI_2 \end{cases}$$


$$\begin{cases} f_1 - f_2 = 2RI_1 - RI_2 & [1] \\ f_2 - f_3 = -RI_1 + 3RI_2 & [2] \end{cases}$$

$$[1] + 2[2] \quad f_1 + f_2 + f_3 = 5RI_2 \Rightarrow I_2 = \frac{f_1 + f_2 + f_3}{5R} = 2.2 \cdot 10^{-3} \text{ A}$$

$$3 \cdot [1] + [2] \quad 3f_1 - 2f_2 - f_3 = 5RI_1 \Rightarrow I_1 = \frac{3f_1 - 2f_2 - f_3}{5R} = 2.6 \cdot 10^{-3} \text{ A}$$

$$\Delta V_{AB} = RI_2 = 2.2 \text{ V}$$
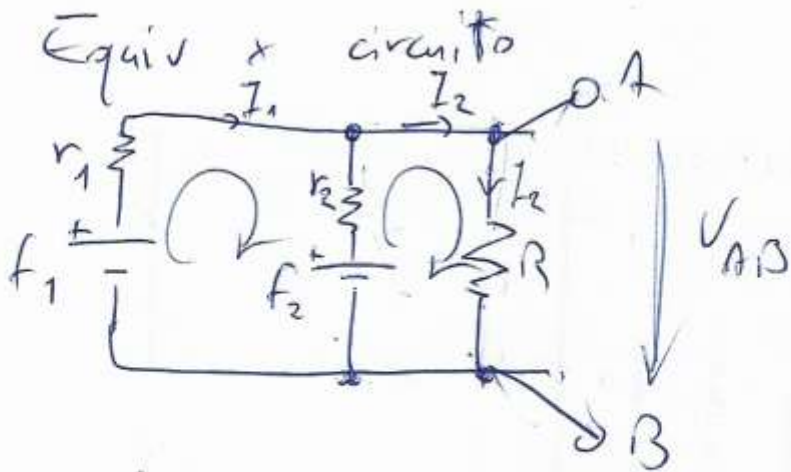
$$\Delta V_{CD} = R(I_1 - I_2) = 0.4 \text{ V}$$



$$f_1 = 3V$$

$$f_2 = 12V$$

$$r_1 = 5\Omega$$

$$r_2 = 3\Omega$$

$$R = 150\Omega$$


$$\begin{cases} f_1 - f_2 = r_1 I_1 + r_2 (I_1 - I_2) \\ f_2 = r_2 (I_2 - I_1) + R I_2 \end{cases}$$

$$f_1 = r_1 I_1 + R I_2 \Rightarrow I_1 = \frac{f_1 - R I_2}{r_1}$$

$$f_2 = -r_2 \frac{f_1 - R I_2}{r_1} + (r_2 + R) I_2$$



$$I_2 = \frac{r_2 f_1 + r_1 f_2}{r_1 r_2 + r_1 R + r_2 R} = 71.6 \mu A$$

$$V_{eq} = V_{AB} = R I_2 = 10.74 V$$

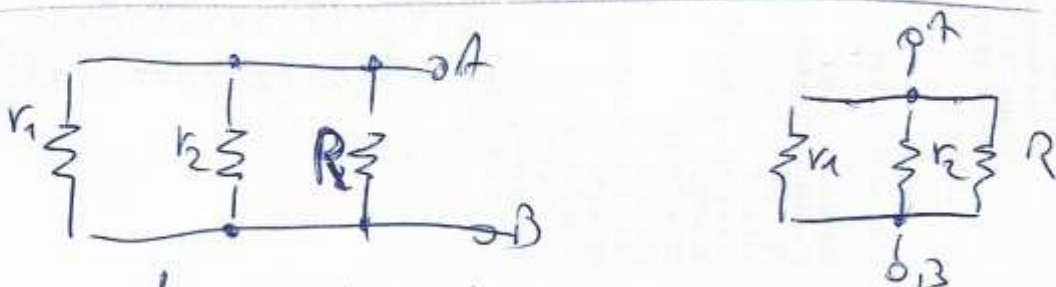


$$\frac{1}{R_{eq}} = \frac{1}{r_1} + \frac{1}{r_2} + \frac{1}{R} \Rightarrow$$
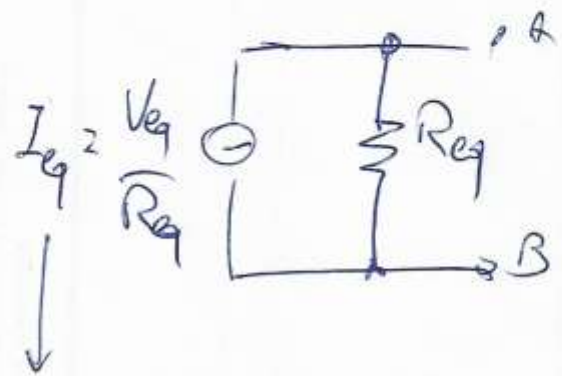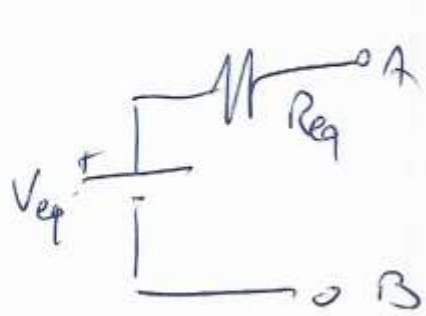
$$R_{eq} = \frac{r_1 r_2 R}{r_1 r_2 + r_1 R + r_2 R} = 1.85 \Omega$$



$$= \frac{r_2 r_1 + r_1 r_2}{r_1 r_2} = \frac{r_1}{r_1} + \frac{r_2}{r_2}$$


Scarica di un condensatore

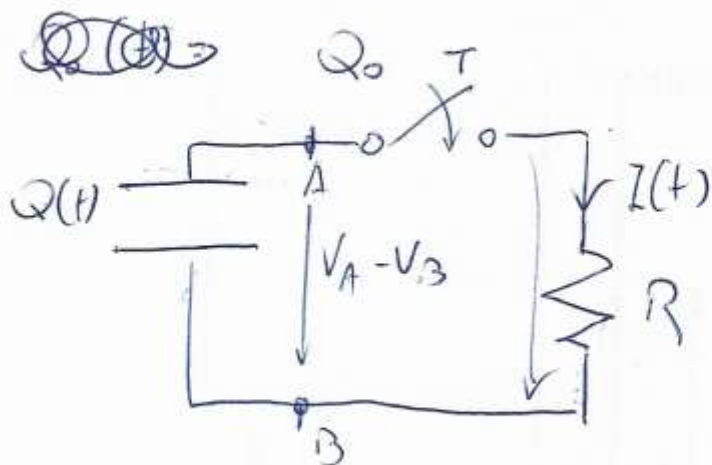

T chiuso $t = \phi$

$$\left\{ \begin{aligned} Q(t=0) &= Q_0 \\ V_0 &= Q_0/C \\ I_0 &= V_0/R \end{aligned} \right.$$
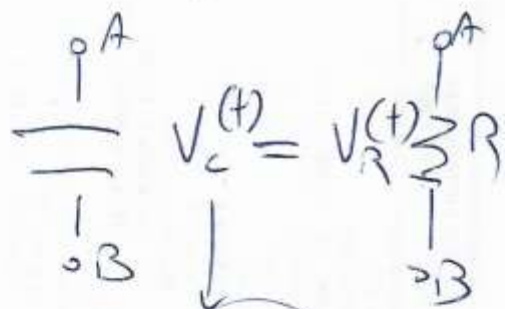
$$\left. \begin{aligned} t \rightarrow \infty \\ V_0 &= \frac{Q_0}{C} \\ I_0 &= \phi \end{aligned} \right\}$$



$$\frac{Q(t)}{C} = I(t) R$$

$$I(t) = \frac{dq}{dt}$$

~~$Q = q$~~

$$Q = -q$$

$$I(t) = -\frac{dQ(t)}{dt}$$

$$\frac{Q(t)}{C} = -\frac{dQ(t)}{dt} R$$

$$\frac{1}{RC} \int dt = -\int \frac{dQ}{Q}$$

$$\frac{1}{RC} t = -\log Q(t) + \log A = -\log \left(\frac{Q(t)}{A} \right)$$

$$Q(t) = A e^{-t/RC}$$

$$Q(t=\phi) = \boxed{Q_0 = A} \Rightarrow Q(t) = Q_0 e^{-t/RC}$$

$$\tau = RC \longrightarrow 100 \text{ pF/m} \quad 6 + 2 - 12$$

$$1 \text{ k}\Omega$$

$$10^6 \cdot 10^2 \cdot 10^{-12} = 10^{-4} \text{ s}$$

$$c \approx 10^8 \text{ m/s}$$

$$10 \text{ ns}$$


$$I(t) = -\frac{dQ}{dt} = \frac{Q_0}{RC} e^{-t/RC} = \frac{V_0}{R} e^{-t/RC} = I_0 e^{-t/RC}$$

$$U_j = \int_{\phi}^{+\infty} R I^2(t) dt = \frac{Q_0^2}{RC} \int_{\phi}^{+\infty} e^{-2t/RC} dt = -\frac{Q_0^2}{RC} \frac{RC}{2} \left[e^{-2t/RC} \right]_{\phi}^{+\infty}$$

$$= \frac{1}{2} \frac{Q_0^2}{C} = U_{oc}$$

$$U_j(\phi - t^*) = \frac{1}{2C} [Q_0^2 - Q^2(t^*)]$$

$$U_c(t^*) = \frac{Q^2(t^*)}{2C}$$

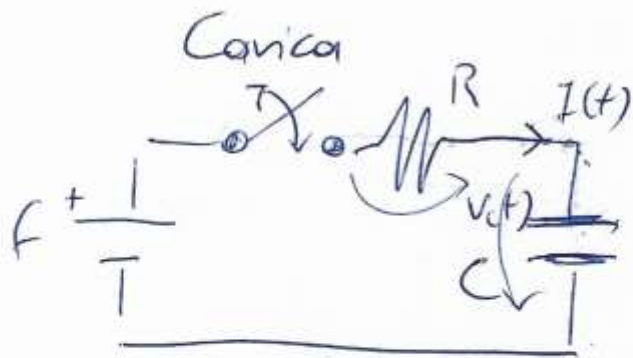

$t = \phi$ chiude circuito

$$f = V_c(t) + RI(t) = \frac{Q(t)}{C} + R \frac{dQ(t)}{dt}$$

$$I = \frac{dq}{dt} = \frac{dQ}{dt}$$



$$fC - Q(t) = RC \frac{dQ}{dt} \sim$$

$$\left[\frac{dt}{RC} = \frac{dQ}{fC - Q(t)} \right]$$

$t = \phi$

$$Q_0 = \phi$$

$$V_0 = \phi$$

$$I_0 = f/R$$

$t = \infty$

$$Q_{\infty} = fC$$

$$V_{\infty} = f$$

$$I_{\infty} = \phi$$

$$y = fC - Q$$

$$dy = -dQ$$

$$\frac{dt}{RC} = -\frac{dy}{y} \Rightarrow y(t) = Ae^{-t/RC}$$

$$\tau = RC$$

$$fC - Q(t) = Ae^{-t/RC}$$


$$Q(t) = fC - Ae^{-t/RC}$$


c.ii. $Q_0 = \phi = fC - A \Rightarrow A = fC$

$$Q(t) = Q_{\infty} (1 - e^{-t/RC}) = fC (1 - e^{-t/RC})$$

$$V_c(t) = \frac{Q(t)}{C} = f (1 - e^{-t/RC})$$
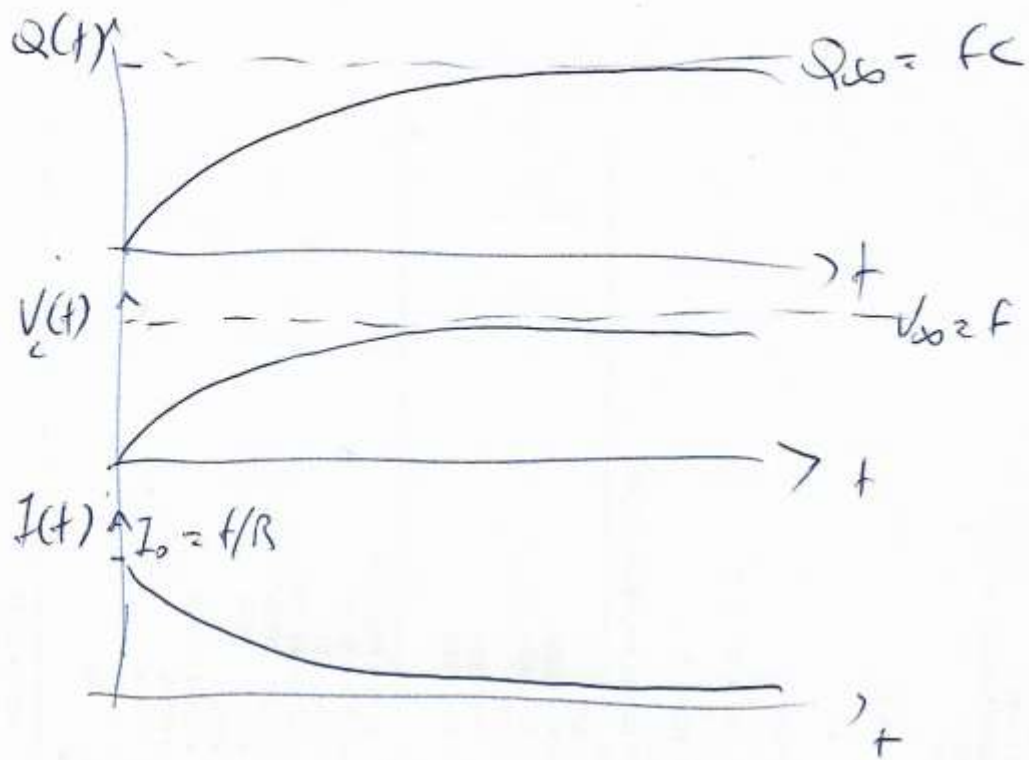
$$I(t) = \frac{dQ}{dt} = fC \frac{1}{RC} e^{-t/RC} = \frac{f}{R} e^{-t/RC} = I_0 e^{-t/RC}$$



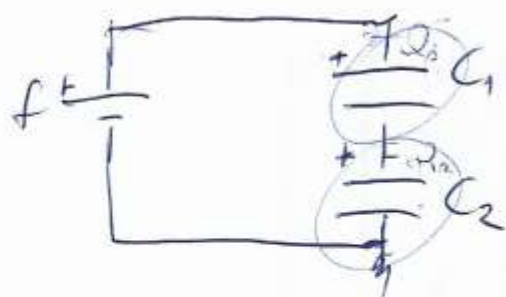


$$Q_0 = V_1 C_1 = V_2 C_2$$

$$f = V_1 + V_2 = Q_0 \left(\frac{1}{C_1} + \frac{1}{C_2} \right) =$$

$$= Q_0 \cdot \frac{1}{C_s} = Q_0 \frac{C_1 + C_2}{C_1 C_2}$$

$$Q_0 = f \frac{C_1 C_2}{C_1 + C_2} = f C_s$$

$$U_0 = \frac{1}{2} \frac{Q_0^2}{C_s}$$

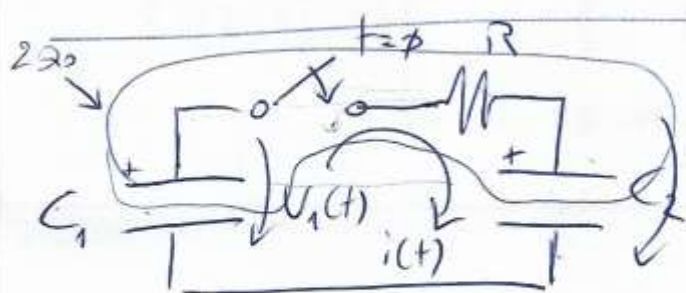

$$V_{10} = V_1(t=p) = \frac{Q_0}{C_1}$$

$$V_{20} = V_2(t=p) = \frac{Q_0}{C_2}$$

$$V_1(t) - V_2(t) = R i(t)$$

$$\frac{Q_1(t)}{C_1} - \frac{Q_2(t)}{C_2} = R i(t) \quad \leftarrow \frac{d}{dt}$$

$$i(t) = - \frac{dQ_1(t)}{dt} = \frac{dQ_2(t)}{dt}$$

$$\frac{1}{C_1} \frac{dQ_1}{dt} - \frac{1}{C_2} \frac{dQ_2}{dt} = R \frac{di}{dt}$$

$$-\frac{i(t)}{C_1} - \frac{i(t)}{C_2} = R \frac{di(t)}{dt}$$

$$-\frac{1}{RC_s} i(t) = \frac{di(t)}{dt} \rightarrow i(t) = A e^{-t/RC_s}$$

$$\textcircled{R} Ri(\varphi) = \left(\frac{1}{C_1} - \frac{1}{C_2} \right) Q_0 = V_{10} - V_{20} = RA$$

$$A = \frac{V_{10} - V_{20}}{R} (= I_0)$$

$$i(t) = \frac{V_{10} - V_{20}}{R} e^{-t/RC_s}$$

$$\frac{dQ_2(t)}{dt} = i(t) \quad Q_2(t) = \int_{\varphi}^t i(t') dt' = -\frac{V_{10} - V_{20}}{R} RC_s e^{-t/RC_s} + k$$

$$Q_2(t=\varphi) = -C_s(V_{10} - V_{20}) + k = Q_0$$

$$\Rightarrow k = Q_0 + C_s(V_{10} - V_{20})$$

$$\Rightarrow Q_2(t) = Q_0 + C_s(V_{10} - V_{20})(1 - e^{-t/RC_s})$$

$$Q_{2\infty} = Q_0 + C_s(V_{10} - V_{20}) = 2Q_0 \frac{C_2}{C_1 + C_2}$$

$\swarrow \frac{Q_0}{C_1} \quad \nwarrow \frac{Q_0}{C_2}$

$$Q_1(t) + Q_2(t) = Q_{10} + Q_{2\infty} = \underline{\underline{2Q_0}}$$

$$Q_1(t) = \textcircled{2} Q_0 - Q_2(t)$$

$$Q_1(t) = Q_0 - C_2 (V_{10} - V_0) (1 - e^{-t/RC_2})$$

$$Q_{1\infty} = \dots = 2Q_0 \frac{C_1}{C_1 + C_2}$$

$$V_1(t) = \frac{Q_1(t)}{C_1}$$

$$V_{1\infty} = \frac{Q_{1\infty}}{C_1} = \frac{2Q_0}{C_1 + C_2} \downarrow \textcircled{=}$$

$$V_2(t) = \frac{Q_2(t)}{C_2}$$

$$V_{2\infty} = \frac{Q_{2\infty}}{C_2} = \frac{2Q_0}{C_1 + C_2} \uparrow$$

$$U_f = \frac{1}{2} \frac{(2Q_0)^2}{C_1} = \frac{1}{2} \frac{4Q_0^2}{C_1 + C_2} = \frac{2Q_0^2}{C_1 + C_2} < U_0$$