

Ohmici





$$\Delta V = RI$$


$$\hookrightarrow \vec{E} = \rho \vec{j}$$

$$R = \rho \frac{L}{S}$$

parametri concentrati

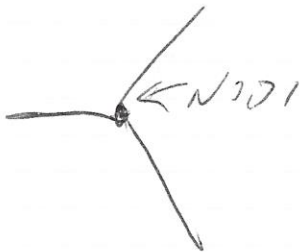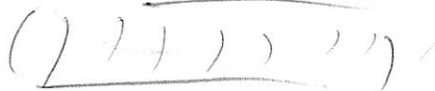

$$\sum_i I_i = 0$$

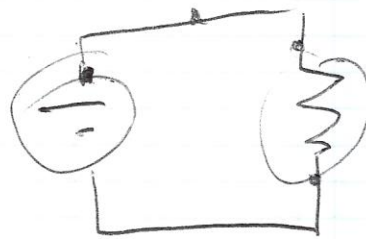

ALTE PARALLE

$$\sum_i f_i = \sum_j R_j I_j$$

I K.





$$P_a = fI \rightarrow$$

(11-1)

Ponte di Wheatstone

2

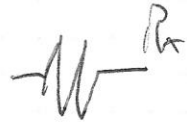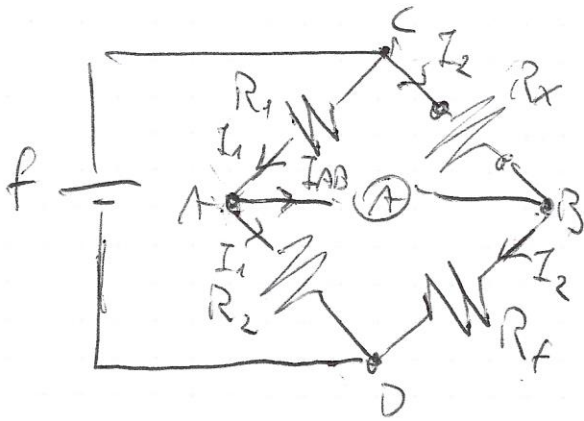

$$I_{AB} = \phi$$

$$V_A = V_B$$

$$V_C - V_A = V_C - V_B$$

$$R_f I_1 = R_x I_2$$

$$\frac{R_1}{R_2} = \frac{R_x}{R_f}$$

$$V_A - V_D = V_B - V_D$$

$$R_2 I_1 = R_f I_2$$



$$R_f = R_x \cdot \frac{R_1}{R_2}$$

quando $I_{AB} = \phi$

Metodo delle correnti di maglia

3

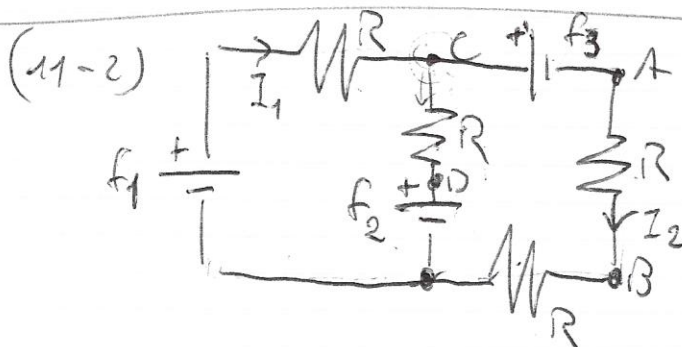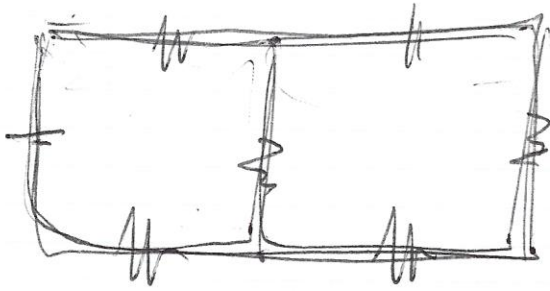maglie indipendenti = # rami - # nodi + 1



ΔV_{AB}

ΔV_{CD}

$f_1 = 12\text{ V}$

$f_2 = 9\text{ V}$

$f_3 = 5\text{ V}$

$R = 1\text{ k}\Omega$

$$\begin{cases} f_1 - f_2 = RI_1 + R(I_1 - I_2) \\ f_2 - f_3 = R(I_2 - I_1) + RI_2 + RI_2 \end{cases}$$

$$\begin{cases} f_1 - f_2 = 2RI_1 - RI_2 & [1] \\ f_2 - f_3 = -RI_1 + 3RI_2 & [2] \end{cases}$$

$[1] + 2 \cdot [2] \quad f_1 + f_2 - 2f_3 = 5RI_2$

$I_2 = (f_1 + f_2 - 2f_3) / 5R = 2.2\text{ mA}$


$3[1] + [2]$

$I_1 = (3f_1 - 2f_2 - f_3) / 5R = 2.6\text{ mA}$

$\Delta V_{AB} = RI_2 = 2.2\text{ V}$

$\Delta V_{CD} = R(I_1 - I_2) = 0.4\text{ V}$

(41-3)

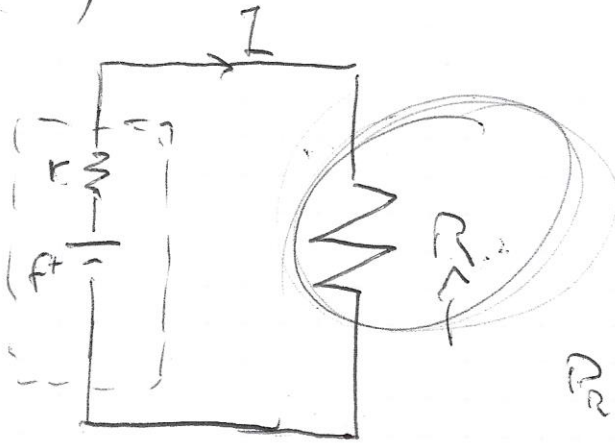

$$f = rI + RI = (r+R)I$$

$$I = \frac{f}{r+R}$$

$$P_R = RI^2 = R \left(\frac{f}{r+R} \right)^2 \quad \text{--- } \phi$$

$$\frac{dP}{dR} = f^2 \cdot \frac{(r+R)^2 - 2R(r+R)}{(r+R)^4} = \dots =$$

$$= \frac{r^2 - R^2}{(r+R)^4} = \frac{r-R}{(r+R)^3} = \phi \quad \boxed{R=r}$$


~~$P = \frac{f^2 R}{(r+R)^2}$~~

$$P_R = R \left(\frac{f}{r+R} \right)^2 = \frac{f^2}{4r} \quad \text{--- } R=r$$

$$\eta = \frac{P_R}{P_T} = \frac{P_R}{P_r + P_R} = \frac{RI^2}{(r+R)I^2} = \frac{R}{r+R}$$


$R \rightarrow \infty$
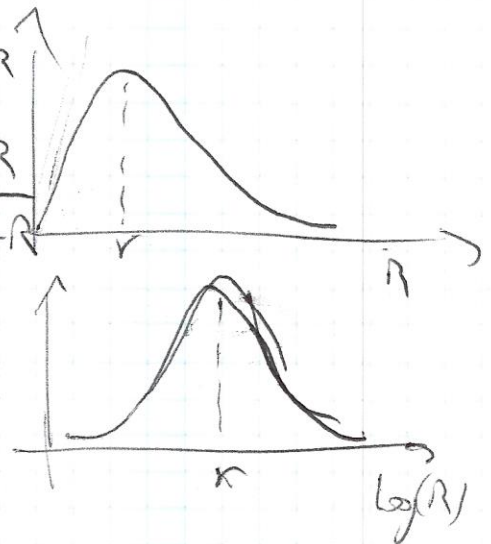
$$\eta = \frac{1}{2} \quad R=r \quad 50\%$$



Teoremi di Thévenin e di Norton

5

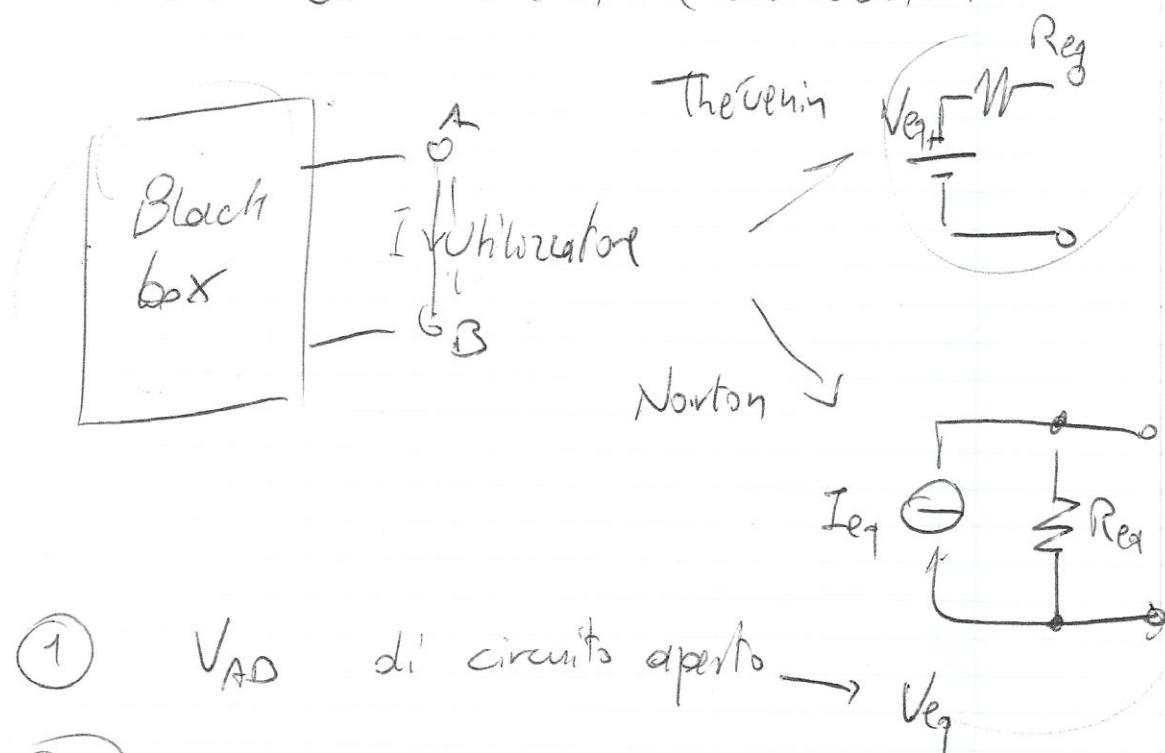



\hookrightarrow equiv. R_{eq} a generatori disattivati

g. tensione \rightarrow c.c.

g. corrente \rightarrow c.a.

$$I_{\text{eq}} = \frac{V_{\text{eq}}}{R_{\text{eq}}}$$

6

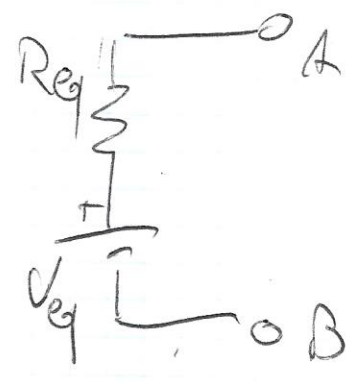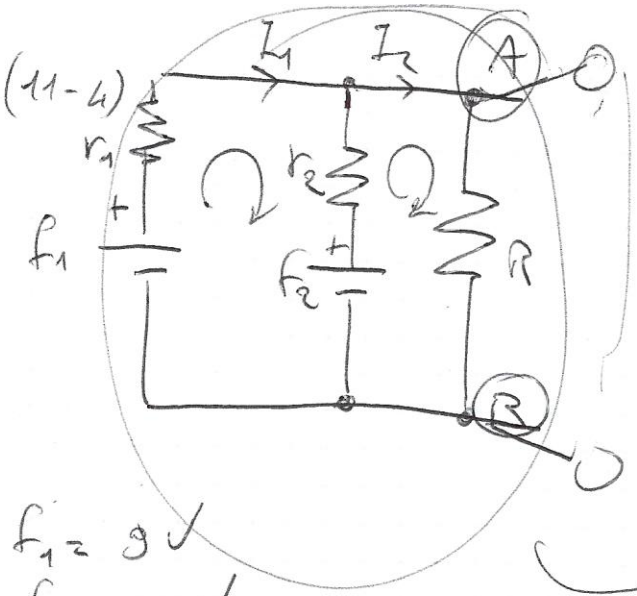

$f_1 = 9V$
 $f_2 = 12V$
 $r_1 = 5\Omega$
 $r_2 = 3\Omega$
 $R = 15\Omega$

$$\begin{cases} f_1 - f_2 = (r_1 + r_2) I_1 - r_2 I_2 \\ f_2 = -r_2 I_1 + (r_2 + R) I_2 \end{cases}$$



$$f_1 = r_1 I_1 + R I_2$$

$$I_1 = \frac{f_1 - R I_2}{r_1}$$

$$f_2 = -r_2 \frac{f_1 - R I_2}{r_1} + (r_2 + R) I_2$$

$$I_2 = \frac{r_2 f_1 + R f_2}{(r_1 r_2 + r_1 R + r_2 R)} = 71.6 \text{ mA}$$
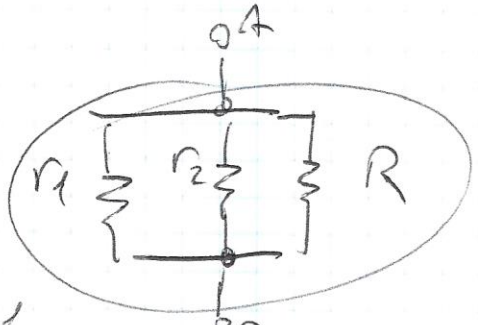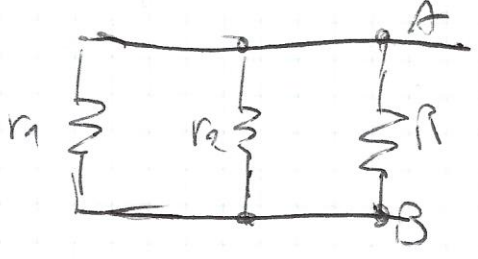
$$V_{eq} = \Delta V_{ABca} = R I_2 = 10.74 V$$




$$\frac{1}{R_{eq}} = \frac{1}{r_1} + \frac{1}{r_2} + \frac{1}{R}$$

$$R_{eq} = \frac{r_1 r_2 R}{r_1 r_2 + r_1 R + r_2 R} = 1.85 \Omega$$


$$I_{eq} = \frac{V_{eq}}{R_{eq}} = 5.81 A$$

Transitori lenti

7

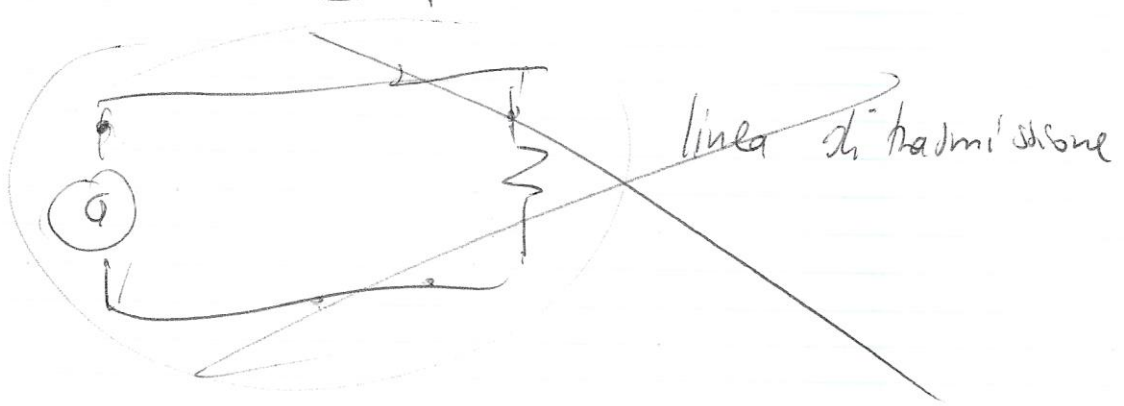

Scarica di un condensatore (12-1)

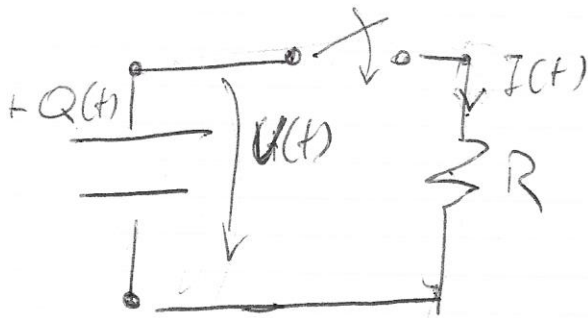

$$Q_0$$

$$t = \phi \quad Q(\phi) = Q_0$$

$$V(t) = R I(t)$$

~~$$i = \frac{dq}{dt} = \frac{dQ}{dt}$$~~

$$\frac{Q(t)}{C} = -R \frac{dQ(t)}{dt}$$

$$I(t) = - \frac{dQ(t)}{dt}$$

$$\begin{cases} V_0 = \frac{Q_0}{C} \\ I_0 = \frac{V_0}{R} \end{cases} \quad \begin{cases} V_{\infty} = \frac{Q_{\infty}}{C} = \phi \\ I_{\infty} = \phi \end{cases}$$

$$\frac{1}{RC} \int dt = - \int \frac{dQ(t)}{Q(t)}$$

$$\frac{1}{RC} t = -\log Q(t) + A' = -\log(Q(t)/A)$$

$$A' = \log A$$

$$Q(t) = A e^{-t/RC}$$

$$Q(t = \phi) = Q_0 = A$$

$$\Rightarrow \boxed{Q(t) = Q_0 e^{-t/RC}} \quad \tau = RC$$

$$I(t) = -\frac{dQ}{dt} = \frac{Q_0}{RC} e^{-t/RC} = \left(\frac{V_0}{R}\right) e^{-t/RC} \quad \text{⑧}$$

$I_0 = \frac{V_0}{R}$


$$Q_j = \int_0^{+\infty} R I(t)^2 dt = \frac{Q_0^2}{RC^2} \int_0^{+\infty} e^{-2t/RC} dt$$

$$= - \frac{Q_0^2}{RC^2} \left[\frac{RC}{2} e^{-2t/RC} \right]_0^{+\infty} = \frac{1}{2} \frac{Q_0^2}{C} = U_C(t=0)$$

$$Q_j(t^*) = \frac{1}{2C} [Q_0^2 - Q(t^*)^2]$$

$$U_C(t^*) = \frac{1}{2} \frac{Q(t^*)^2}{C}$$

(12-2)

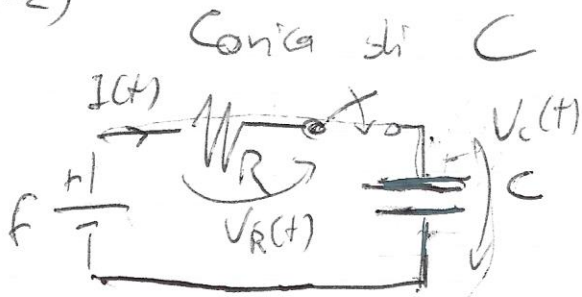

$t=0$ chiusura

9

$$f = V_C(t) + V_R(t) = \frac{Q(t)}{C} + RI(t)$$

$$f = \frac{Q(t)}{C} + R \frac{dQ(t)}{dt}$$

$$\frac{dt}{RC} = \frac{dQ(t)}{fC - Q(t)}$$

$$y = fC - Q$$

$$\frac{dy}{dQ} = -1 \quad dy = -dQ$$

$$\frac{dt}{RC} = -\frac{dy}{y} \quad \rightarrow \quad y(t) = Ae^{-t/RC} \quad \tau = RC$$

$$\left\{ \begin{array}{l} Q_0 = 0 \\ V_{C0} = 0 \\ I_0 = f/R \end{array} \right. \quad \left\{ \begin{array}{l} Q_{\infty} = fC \\ V_{C\infty} = f \\ I_{\infty} = 0 \end{array} \right.$$


$$fC - Q(t) = Ae^{-t/RC} \quad \rightarrow \quad Q(t) = fC - Ae^{-t/RC}$$

$$Q(t=0) = 0 = fC - A \quad \Rightarrow \quad A = fC$$

$$Q(t) = fC (1 - e^{-t/RC})$$

$$V(t) = \frac{Q(t)}{C} = f(1 - e^{-t/RC})$$
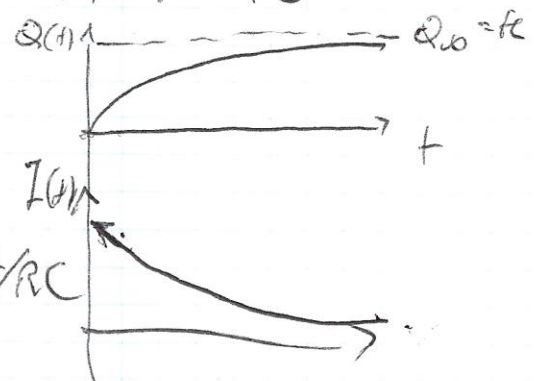
$$I(t) = \frac{dQ}{dt} = \frac{f}{R} e^{-t/RC} = I_0 e^{-t/RC}$$




$$U_g = \int_0^{+\infty} W_g(t) dt = \int_0^{+\infty} f \cdot I(t) dt = \frac{f^2}{R} \int_0^{+\infty} e^{-t/RC} dt = -f^2 C \left[e^{-t/RC} \right]_0^{+\infty} = Cf^2 \quad (10)$$

$$U_c = \frac{1}{2} CV_{\infty}^2 = \frac{1}{2} Cf^2$$

$$U_j = \int_0^{+\infty} RI^2(t) dt = \frac{f^2}{R} \int_0^{+\infty} e^{-2t/RC} dt = \frac{1}{2} Cf^2$$

$$I \times f = \frac{Q(t)}{C} + RI(t) + I$$

$$fI = \frac{Q(t) I(t)}{C} + RI^2(t)$$

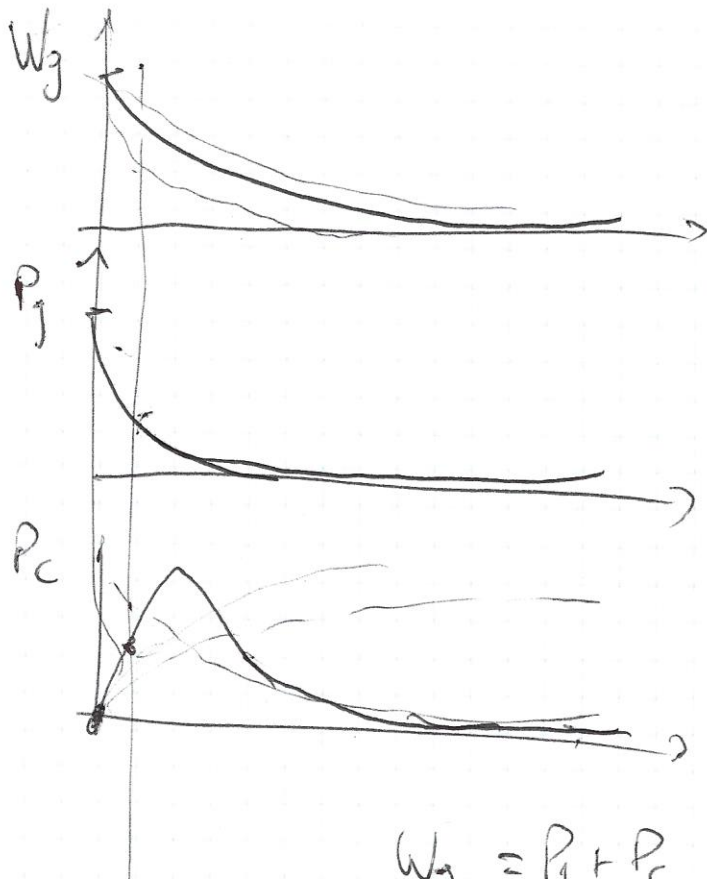

$$W_g = fI = fI_0 e^{-t/RC}$$

$$P_j = RI^2 = RI_0^2 e^{-2t/RC}$$

$$P_c = \frac{1}{2} Q(t) \cdot I(t)$$

$$W_g = P_j + P_c$$