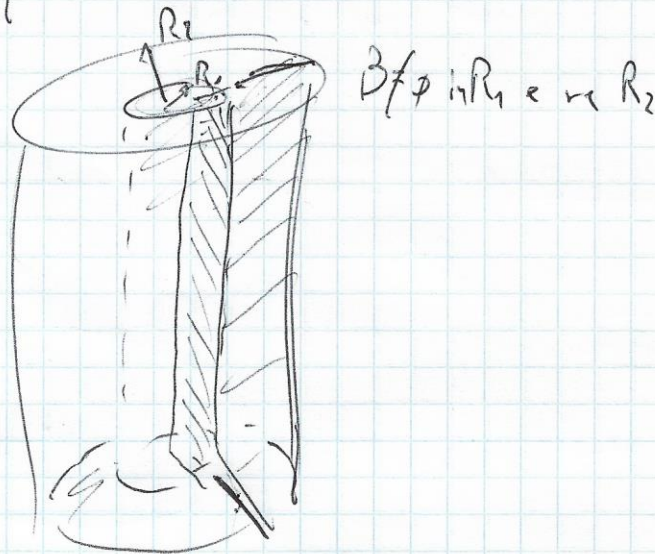



(18-6) ripete

(1)



Cond. centrale pieno

$I \rightarrow j \bar{u} R_1^2$

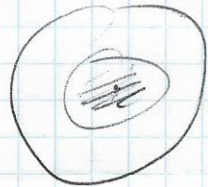

$B(r) = \frac{\mu_0 I}{2\pi R_1^2} r \quad \forall r < R_1$

$r < R_1$

$d\Phi_{in} = B(r) l dr$

$L = \frac{\Phi}{I}$

$L_{in} \text{ no } I \text{ ma } I \left(\frac{r}{R_1}\right)^2$

$d\Phi_{in} = B(r) dr \cdot \left(\frac{r}{R_1}\right)^2$

$\Phi_{in} = \int d\Phi_{in} = \int_0^{R_1} \frac{\mu_0 I}{2\pi R_1^2} r^3 l dr = \frac{\mu_0 I l}{2\pi R_1^4} \left[\frac{r^4}{4} \right]_0^{R_1} \Rightarrow$


$\Phi_{in} = \frac{\mu_0 I l}{8\pi}$

$L_{in,u} = \frac{\Phi_{in}}{lI}$

$L_{qu} = \frac{\Phi_{in}}{lI} + \frac{\Phi_{out}}{lI} = \frac{\mu_0}{8\pi} \left[\frac{1}{4} + \log \frac{R_2}{R_1} \right]$

(18-3)

②

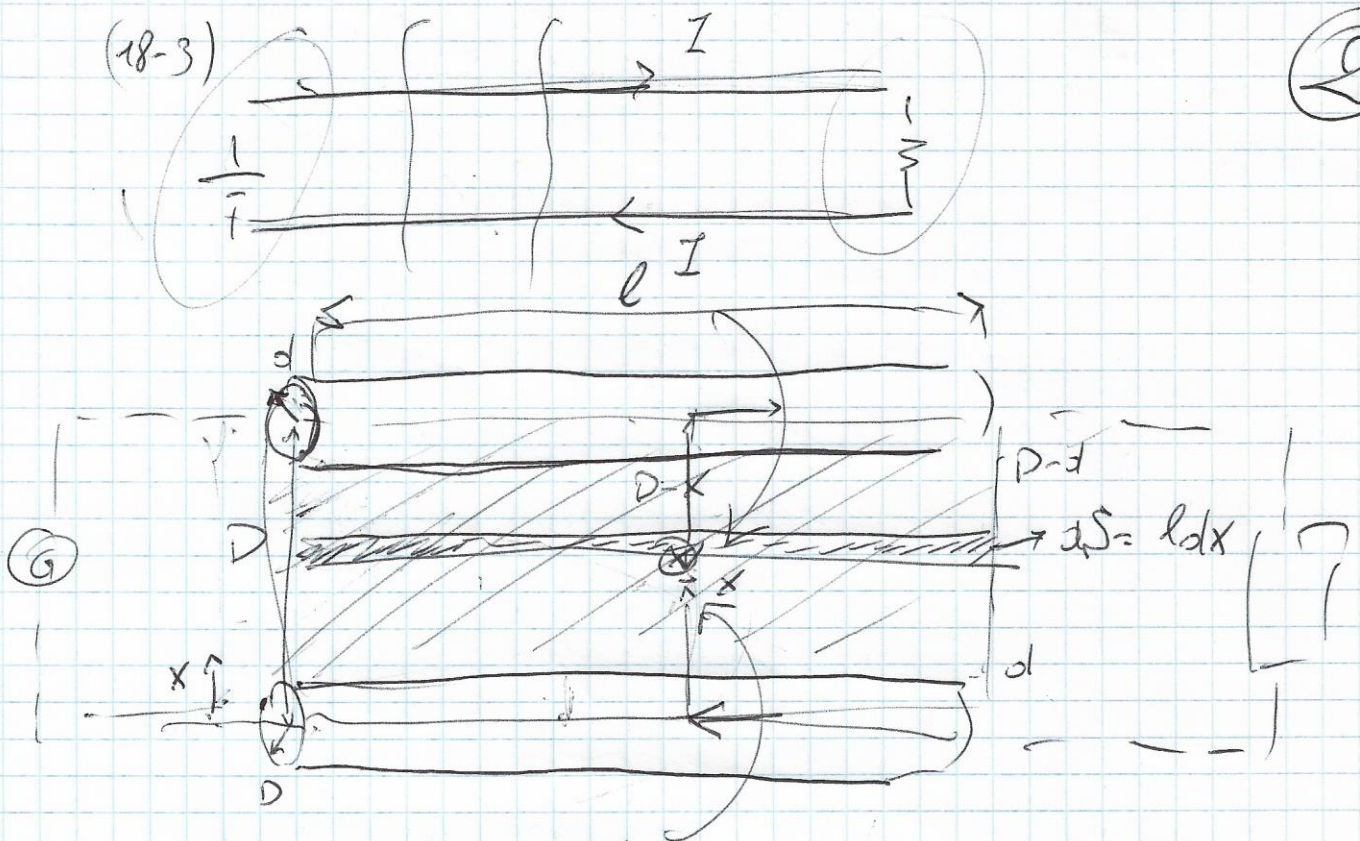

$$B_0(x) = \frac{\mu_0 I}{2\pi x} + \frac{\mu_0 I}{2\pi(D-x)} \quad d\phi = B_0(x) dS = B_0(x) l dx$$

$$\phi(\vec{B}_0) = \frac{\mu_0 I}{2\pi} \int_d^{D-d} \left[\frac{1}{x} + \frac{1}{D-x} \right] l dx = \frac{\mu_0 I l}{2\pi} \left[\log x + \log(D-x) \right]_d^{D-d}$$


$$= \dots \phi = \frac{\mu_0 I l}{2\pi} \log \left(\frac{D-d}{d} \right) \quad \frac{2}{1} \log \left(\frac{D}{d} \right)$$

$$L_{0,u} = \frac{\phi}{I l} = \frac{\mu_0}{2\pi} \log \left(\frac{D-d}{d} \right)$$

Circuiti con L

3

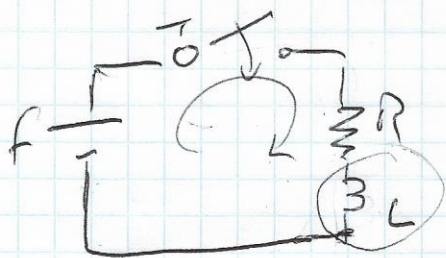Transitorio di chiusura di circ. RL (18-5)



t > 0 switch on

$$\Phi_a = LI$$

$$f_a = - \frac{d\Phi_a}{dt} = -L \frac{dI}{dt}$$

$$f + f_a = RI$$

$$\hookrightarrow -L \frac{dI}{dt}$$


$$f - L \frac{dI}{dt} = RI$$

$$f = RI + L \frac{dI}{dt}$$

$$\tau = \frac{L}{R}$$

$$I_m = \frac{f}{R}$$
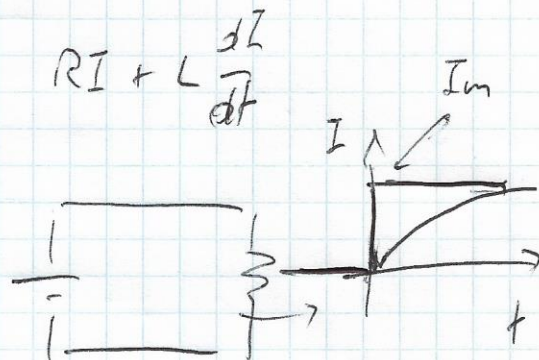
$$\frac{dI}{I - I_m} = - \frac{dt}{\tau}$$



$$\log(I - I_m) = - \frac{t}{\tau} + \log k \quad \phi(I - I_m) = dI$$

$$I(t) - I_m = k e^{-t/\tau}$$

$$I(\phi) = \phi$$

$$\phi - I_m = k$$


$$k = -I_m$$

$$I(t) = I_m (1 - e^{-t/\tau}) = \frac{f}{R} (1 - e^{-t/\tau})$$

$$f_a(t) = -L \frac{dI}{dt} = -f e^{-t/\tau}$$

$$f_a(\phi) = -f$$

$$\tau = L/R$$

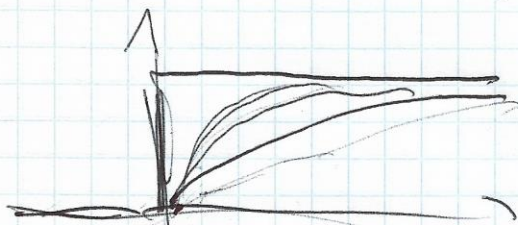

(4)

$$f = RI + L \frac{dI}{dt}$$

energiekomponente?

$$d\mathcal{L} = f dQ = f I dt$$

$$P = \frac{d\mathcal{L}}{dt} = f I$$


$$f I = \underbrace{RI^2}_{P_J} + \underbrace{LI \frac{dI}{dt}}_{P_L}$$

$$d\mathcal{L}_G = f I dt = RI^2 dt + LI dI = dU_R + dU_L$$

$$\mathcal{L}_G = \int_0^t f I dt'$$

$$U_R = \int_0^t RI^2 dt'$$
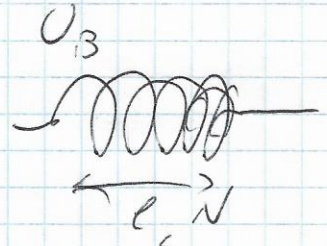
$$U_L = \int_0^{I(t)} LI' dI' = \frac{1}{2} LI^2 \rightsquigarrow$$



$$L \frac{dI}{dt} = \frac{d\Phi}{dt} = N S \frac{dB}{dt}$$

$$\Phi = N S B$$

$$dU_L = LI dI = I \frac{d\Phi}{dt} = N I S dB = \frac{S \mu_0 N^2 I^2}{\mu_0} B dB$$



$$dU_L = \frac{dU_L}{S dl} = \frac{1}{\mu_0} B dB$$

$$u_m = u_L = \int \frac{1}{\mu_0} B \times B = \frac{1}{2\mu_0} B^2$$


$$\Phi = \int \vec{B} \cdot d\vec{S} = \int (\vec{v} \times \vec{A}) \cdot d\vec{S}$$

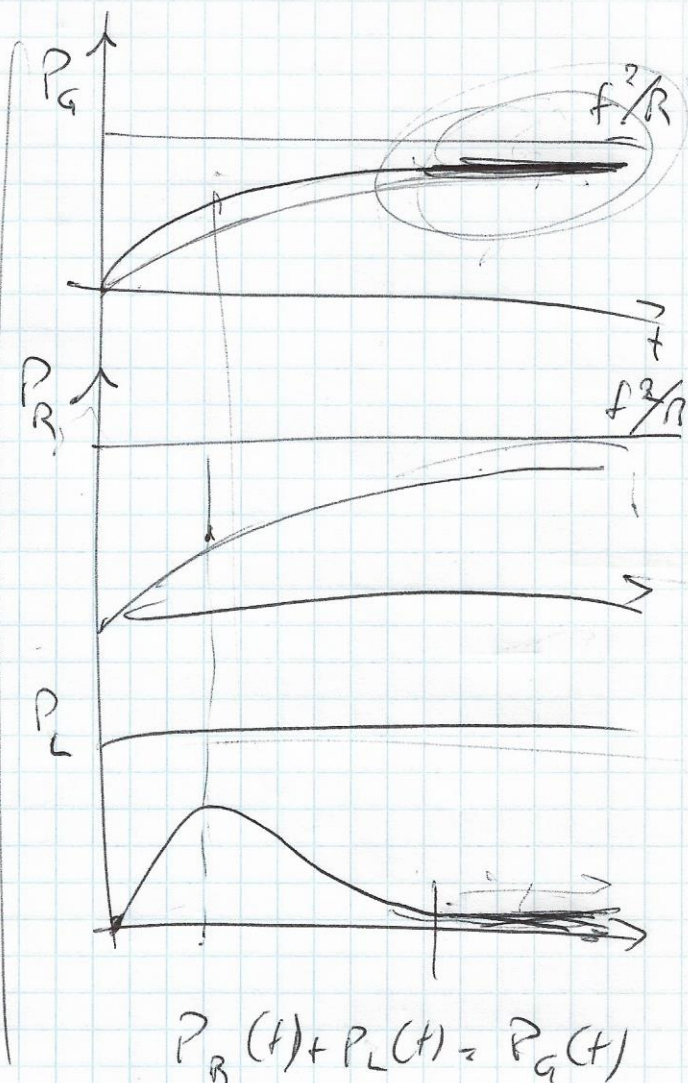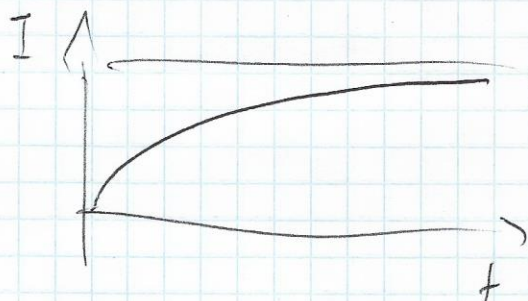(5)

$$U_m = \frac{1}{2\mu_0} \int B^2 dz = \frac{1}{2} \int \vec{A} \cdot \vec{j} dz$$



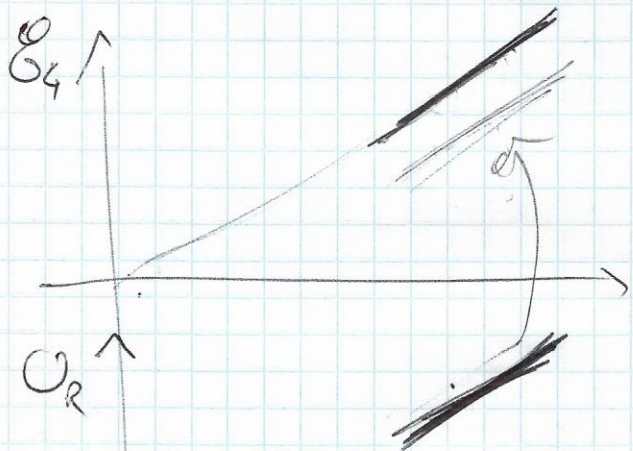
$$RI^2(\infty) = R \frac{f^2}{R^2} = \frac{f^2}{R}$$



(18-6)

6

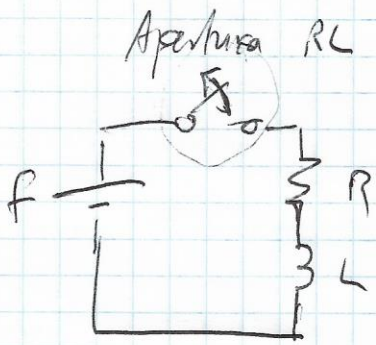

$$R \rightsquigarrow R'$$

$$f - L \frac{dI}{dt} = R'I$$

$$\tau = L/R'$$


$$I(t) = \frac{f}{R'} - k e^{-t/\tau}$$

$$I(\infty) = I_0 = \frac{f}{R} = \frac{f}{R'} - k \rightsquigarrow k = f \left(\frac{1}{R'} - \frac{1}{R} \right) = \frac{f}{R'} - I_0$$

$$I(t) = \frac{f}{R'} - \frac{f}{R'} e^{-t/\tau} + I_0 e^{-t/\tau} = \frac{f}{R'} (1 - e^{-t/\tau}) + I_0 e^{-t/\tau}$$

$$I(t) \approx I_0 e^{-t/\tau} = \frac{f}{R} e^{-t/\tau}$$

Serie

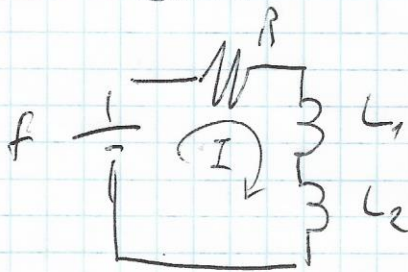

$$f_{L1} = -L_1 \frac{dI}{dt}$$

$$= -f \frac{L_1}{L_1 L_2} e^{-t/\tau}$$

$$f_{L2} = -L_2 \frac{dI}{dt}$$

$$= -f \frac{L_2}{L_1 L_2} e^{-t/\tau}$$

$$f + f_{L1} + f_{L2} = RI$$

$$f - (L_1 + L_2) \frac{dI}{dt} = RI$$

$$L_{eq} \rightsquigarrow f - L_{eq} \frac{dI}{dt} = RI$$


$$I(t) = \frac{f}{R} (1 - e^{-t/\tau})$$

$$L_{eq \text{ serie}} = \sum_n L_n$$

$$\tau = L_{eq}/R = (L_1 + L_2)/R$$

Parallelo di induttanze

(7)

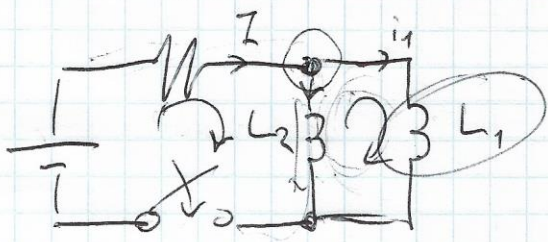

$$f - L_2 \frac{d}{dt} (I - i_1) = RI \quad (1)$$

$$-L_1 \frac{di_1}{dt} - L_2 \frac{d}{dt} (i_1 - I) = 0 \quad (2)$$

$$(2) \quad (L_1 + L_2) \frac{di_1}{dt} = L_2 \frac{dI}{dt}$$

$$\frac{di_1}{dt} = \frac{L_2}{L_1 + L_2} \frac{dI}{dt}$$

Subst. in (1):

$$f - L_2 \frac{dI}{dt} + \frac{L_2^2}{L_1 + L_2} \frac{dI}{dt} = RI$$

$$f = RI + \frac{L_1 L_2}{L_1 + L_2} \frac{dI}{dt} \rightarrow L_{eq}$$

$$\frac{1}{L_{eq}} = \sum \frac{1}{L_n}$$

$$\tau = L_{eq} / R$$

$$I(t) = \frac{f}{R} (1 - e^{-t/\tau})$$


$$i_1(t) = \frac{L_2}{L_1 + L_2} I(t) + \text{constant}$$

$$i_1(t) = \frac{f}{R} \frac{L_2}{L_1 + L_2} (1 - \exp(-t/\tau))$$

in L_2 parte $I - i_1 = \frac{f}{R} \frac{L_1}{L_1 + L_2} (1 - \exp(-t/\tau))$






8


L, C

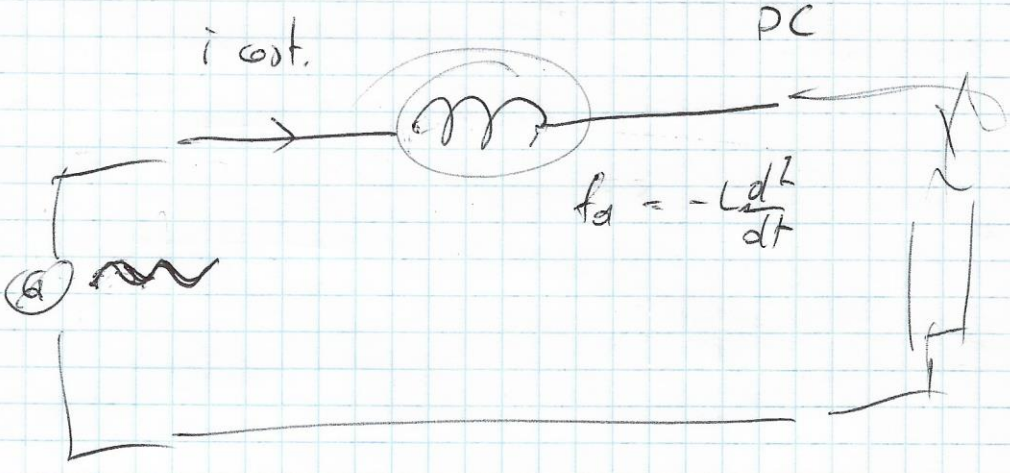

$$\frac{d}{dt} \sin(\omega t) \sim \omega \cos(\omega t)$$

ripple
choke
Low pass filter

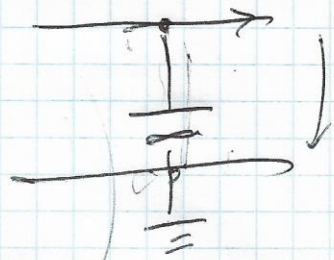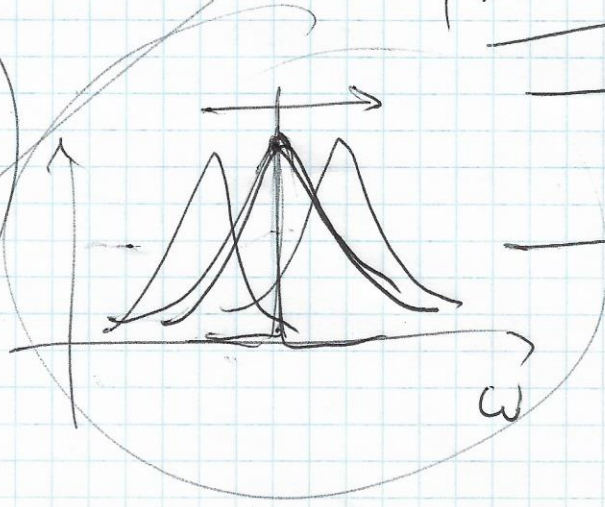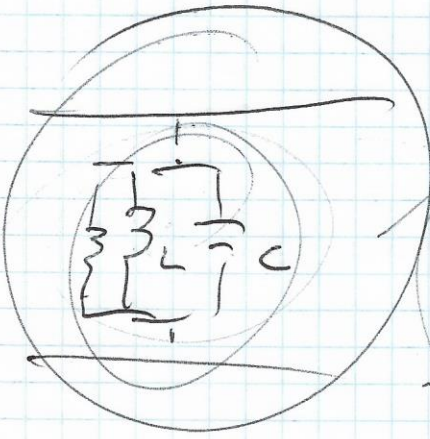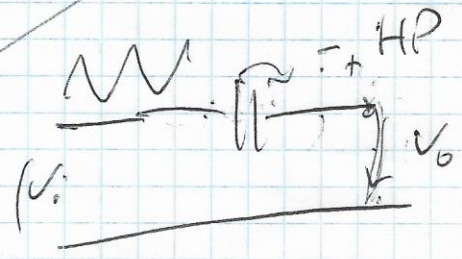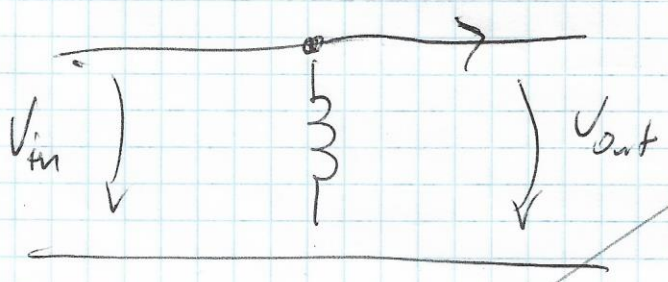

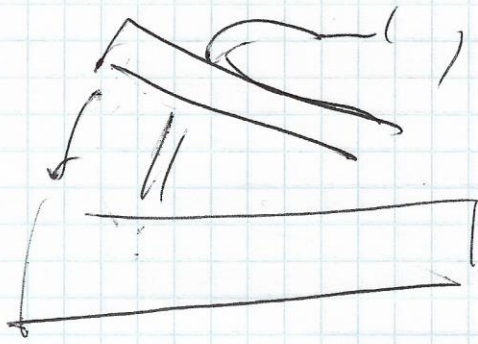

9

Wah pedal, e.g. Crybaby (youtube documentary)



'Cry Baby - The pedal that rocks the world'

also 'I found the first wah demos ever! (1967)'

on the JHS Pedals youtube channel

Tech expl.: 'The technology of wah pedals' on www.gesfex.com